

Name: _____

Class: _____

Due Date: _____

Physics Topic 50 – Internal Resistance

Answer the following questions. The solutions to this worksheet can be found on the YouTube channel Go Physics Go.

1. C: Define *internal resistance* r . Units?


2. C: Define the following variables for the equation $\varepsilon = I(R + r)$. Draw an image to describe this equation.

3. E: A dry cell has an emf of 3.04 V. Its terminal potential drops to zero when a current of 50.0 A passes through it. What is its internal resistance?

4. E: A cell has an emf of 145 V. This means that its terminal voltage is 145 V when no current flows through it. When the terminal potential is 120. V the current through the circuit is 25.0 A.
- a. What is the internal resistance of the cell?
- b. What will be the terminal potential when the current is 12.0 A?
5. E: A cell with internal resistance is connected to a $3.00\ \Omega$ resistor. Determine the internal resistance r of the cell if the current going through it is 2.00 Amps when its \mathcal{E} is 12.0 V.
6. E: A battery with internal resistance is connected to a variable resistor. When the resistor has a resistance R of $12.0\ \Omega$ the current is 2.00 Amps. When the resistor has a resistance R of $6.00\ \Omega$ the current is 3.00 Amps. Determine the emf \mathcal{E} and internal resistance r of the battery.


7. E: While attached to a $2.00\ \Omega$ resistance the terminal voltage of a battery is measured to be $5.20\ \text{V}$. The open circuit voltage of this same battery is measured to be $6.70\ \text{V}$.
- a. What is the internal resistance of the battery?
- b. What will be the maximum current that can be delivered by the battery?
8. E: A battery is known to have an emf of $4.60\ \text{Volts}$ and an internal resistance of $2.20\ \Omega$. What will be the terminal voltage of this battery while connected to a load of $7.80\ \Omega$?

9. E: Consider the circuit below:

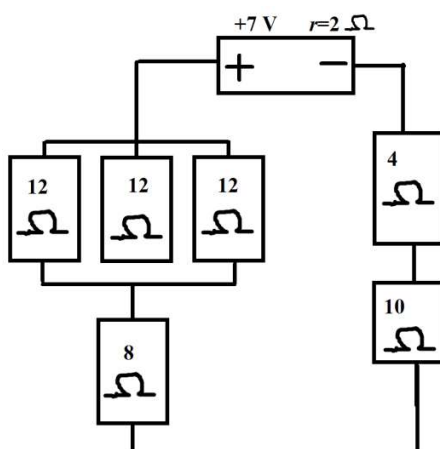

- What is the total resistance of this circuit?
- What will be the total current flowing through this circuit?
- What will be the current flowing through each $12.0\ \Omega$ resistor?
- What will be the voltage drop across each of the $12.0\ \Omega$ resistors?
- What will be the terminal voltage of the battery?
- What will be the voltage drop across the $10.0\ \Omega$ resistor?

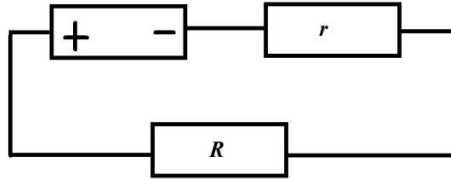10. E: A battery, which has an emf of 6.00 V and an internal resistance $r = 0.500\ \Omega$, is connected to a load which has a resistance of $R = 3.50\ \Omega$.



- a. What will be the current flowing in this circuit?
- b. What will be the voltage drop across the load?
- c. How much power is being supplied by the battery?
- d. How much power is being consumed by the load?
- e. How much power is being consumed by the internal resistance of the battery?
- f. With what efficiency is power being delivered to the load in this circuit?